

Taylor Cowley  
EE 220  
May 24 2016  
Lab 07: Register File


### 1 bit Register Verilog Code

```
module register(dout, din, clk, clr, write);  
    input din;  
    input clk;  
    input clr;  
    input write;  
    output dout;  
  
    wire intermediate;  
  
    FF_DC flip_flop(dout, clk, clr, intermediate);  
    mux_2 mux(intermediate, write, dout, din);  
endmodule
```

### 1-bit Register tcl file

```
isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns  
isim force add clr 1 -time 0 -value 0 -time 50ns  
isim force add write 0 -time 0 -value 1 -time 75ns -value 0 -time 135ns -value 1 -time 145ns -value 0 -time 155ns  
isim force add din 0 -time 0 -value 1 -time 75ns -value 0 -time 115ns -value 1 -time 145ns -value 0 -time 155ns  
run 200ns
```

### 1-bit Register simulation waveform

 

#### 4-bit Register Verilog Code


```
module register_4(dout, din, clk, clr, write);
    input[3:0] din;
    input clk;
    input clr;
    input write;
    output[3:0] dout;

    register r0(dout[0],din[0],clk,clr,write);
    register r1(dout[1],din[1],clk,clr,write);
    register r2(dout[2],din[2],clk,clr,write);
    register r3(dout[3],din[3],clk,clr,write);
endmodule
```

#### 4-bit Register tcl file

```
isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add clr 1 -time 0 -value 0 -time 50ns
isim force add write 0 -time 0 -value 1 -time 75ns -value 0 -time 135ns -value 1 -time 145ns -value 0 -time 155ns
isim force add din 1111 -time 0 -value 1100 -time 75ns -value 0110 -time 115ns -value 1111 -time 145ns -value 1000 -time 155ns
run 200ns
```

#### 4-bit Register simulation waveform

 

#### 2 to 4 Decoder Verilog code


```
module decoder_2_4(in, out);
    input[1:0] in;
    output[3:0] out;

    assign out[3] = in[1] & in[0];
    assign out[2] = in[1] & ~in[0];
    assign out[1] = ~in[1] & in[0];
    assign out[0] = ~in[1] & ~in[0];
endmodule
```

#### 2 to 4 decoder tcl file

```
isim force add in 00 -time 0ns -value 01 -time 10ns -value 10 -time 20ns -value 11 -time 30ns -value 01 -time 40ns
run 50ns
```

#### 2 to 4 decoder simulation waveform

 

## 4x4 Registers Verilog


```
module register_4_4(dout, din, clk, clr, write, address);
    input[3:0] din;
    input clk;
    input clr;
    input write;
    input [1:0] address;
    output[15:0] dout;

    wire [3:0] wr_en, write_enable;
    register_4 r0(dout[3:0], din, clk, clr, write_enable[0]);
    register_4 r1(dout[7:4], din, clk, clr, write_enable[1]);
    register_4 r2(dout[11:8], din, clk, clr, write_enable[2]);
    register_4 r3(dout[15:12], din, clk, clr, write_enable[3]);
    decoder_2_4 decode(address, wr_en);
    // We concat the write signal 4 times to be the same length as wr_en
    assign write_enable = wr_en & {write,write,write,write};
endmodule
```

## 4x4 Registers tcl file

```
isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add clr 1 -time 0 -value 0 -time 50ns
isim force add write 0 -time 0 -value 1 -time 75ns -value 0 -time 95ns -value 1 -time 115ns -value 0 -time 135ns
-value 1 -time 155ns -value 0 -time 175ns -value 1 -time 195ns -value 0 -time 215ns
isim force add din 1111
isim force add address 11 -time 0 -value 10 -time 95ns -value 01 -time 135ns -value 00 -time 195ns
run 300ns
```

## 4x4 registers simulation waveform

 

## 16-4 mux Verilog Code

```
module mux_4(out, sel, in);
    input[3:0] in;
    input[1:0] sel;
    output out;

    wire a_or_b, c_or_d;
    mux_2 M0(a_or_b, sel[0], in[0], in[1]);
    mux_2 M1(c_or_d, sel[0], in[2], in[3]);
    mux_2 M2(out, sel[1], a_or_b, c_or_d);
endmodule
```


```
module mux_16_4(out, sel, in3, in2, in1, in0);
    input[3:0] in3, in2, in1, in0;
    input[1:0] sel;
    output[3:0] out;

    mux_4 bit3(out[3], sel, {in3[3], in2[3], in1[3], in0[3]});
    mux_4 bit2(out[2], sel, {in3[2], in2[2], in1[2], in0[2]});
    mux_4 bit1(out[1], sel, {in3[1], in2[1], in1[1], in0[1]});
    mux_4 bit0(out[0], sel, {in3[0], in2[0], in1[0], in0[0]});
endmodule
```

## 16-4 mux tcl file

```
isim force add in3 1111
isim force add in2 1100
isim force add in1 0011
isim force add in0 0000
isim force add sel 11 -time 0 -value 10 -time 95ns -value 01 -time 135ns -value 00 -time 195ns
run 250ns
```

## 16-4 mux simulation waveform

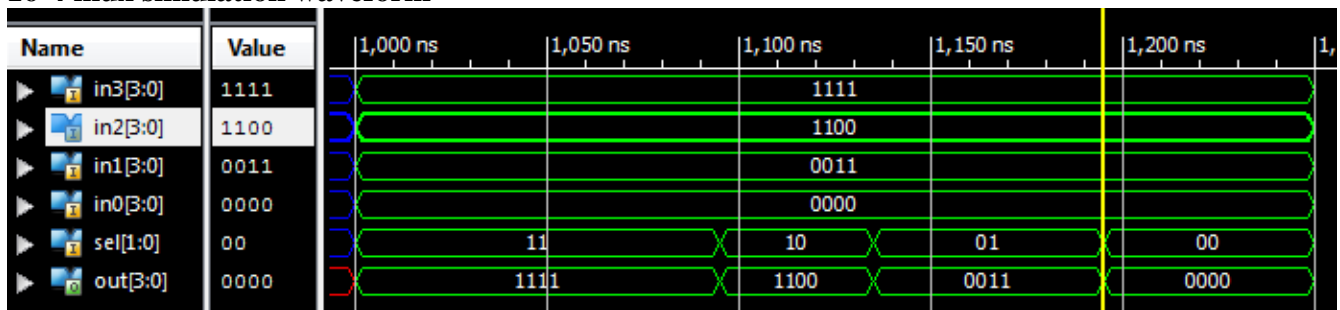

## Complete Register File Verilog Code

```
module register_file_4x4(out, in, write, clr, clk, wr_address, r_address);
    input write, clr, clk;
    input[3:0] in;
    input[1:0] r_address, wr_address;
    output[3:0] out;

    wire[15:0] regout;
    register_4_4 the_register(regout, in, clk, clr, write, wr_address);
    mux_16_4 a_mux(out, r_address, regout[15:12], regout[11:8], regout[7:4], regout[3:0]);
endmodule
```

## Testbench Verilog code

```
module register_file_testbench(Led, sw, btn, clk);
    output[7:0] Led;
    input [7:0] sw;
    input [3:0] btn;
    input clk;

    //module register_file_4x4(out, in, write, clr, clk, wr_address, r_address);
        register_file_4x4 booya(Led[3:0],sw[7:4],btn[3],btn[0],clk,sw[3:2],sw[1:0]);
        buf(Led[7], sw[7]); // Now we have to buffer the output leds to the inputs
        buf(Led[6], sw[6]);
        buf(Led[5], sw[5]);
        buf(Led[4], sw[4]);
    endmodule
```

## Testbench UCF File

```
## clock pin for Nexys 2 Board
NET "clk" LOC = "B8";
```

### ## Leds

```
NET "Led<0>" LOC = "J14";
NET "Led<1>" LOC = "J15";
NET "Led<2>" LOC = "K15";
NET "Led<3>" LOC = "K14";
NET "Led<4>" LOC = "E17";
NET "Led<5>" LOC = "P15";
NET "Led<6>" LOC = "F4";
NET "Led<7>" LOC = "R4";
```

### ## Switches

```
NET "sw<0>" LOC = "G18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW0
NET "sw<1>" LOC = "H18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name = SW1
NET "sw<2>" LOC = "K18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW2
NET "sw<3>" LOC = "K17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW3
NET "sw<4>" LOC = "L14"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW4
NET "sw<5>" LOC = "L13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW5
NET "sw<6>" LOC = "N17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW6
NET "sw<7>" LOC = "R17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW7
```

### ## Buttons

```
NET "btn<0>" LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN0
NET "btn<1>" LOC = "D18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name = BTN1
NET "btn<2>" LOC = "E18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN2
NET "btn<3>" LOC = "H13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN3
```

## Anomalies

I got very confused when adding my UCF file. For one, it added my testbench as simulation only and I had to add it to the implementation as well. And the first time I added the UCF, I accidentally added it to the wrong module. So it disappeared. I had to remove all the modules and add them again one by one to delete the bad UCF and add the right one.