
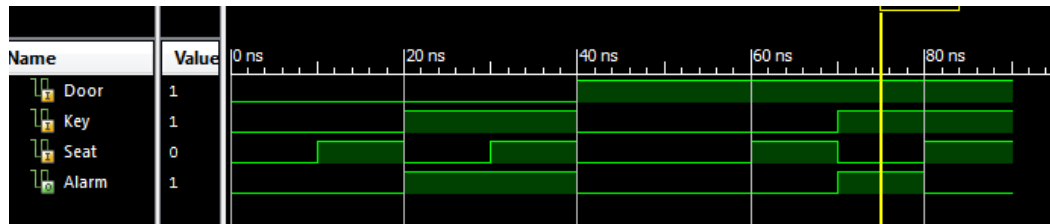
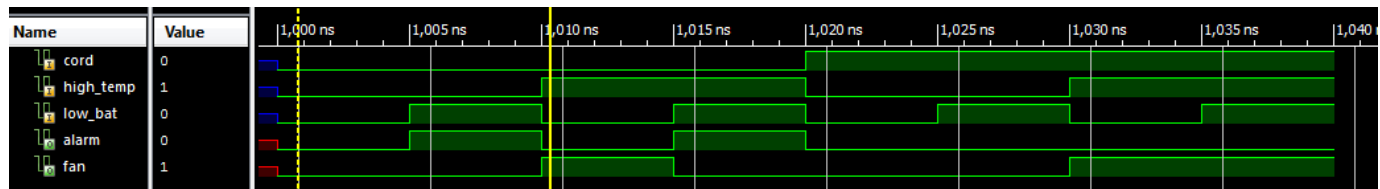



### Car alarm Schematic and simulation waveform


$$(AB+C)'*D*(D+(C+AB)) = F1$$

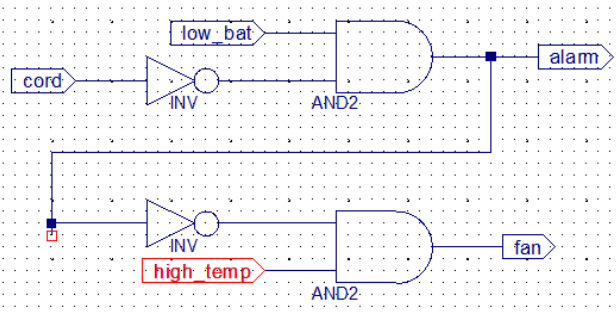2.  $(A + B + C)(A + C + D)(A' + B' + C')(A' + C' + D')$



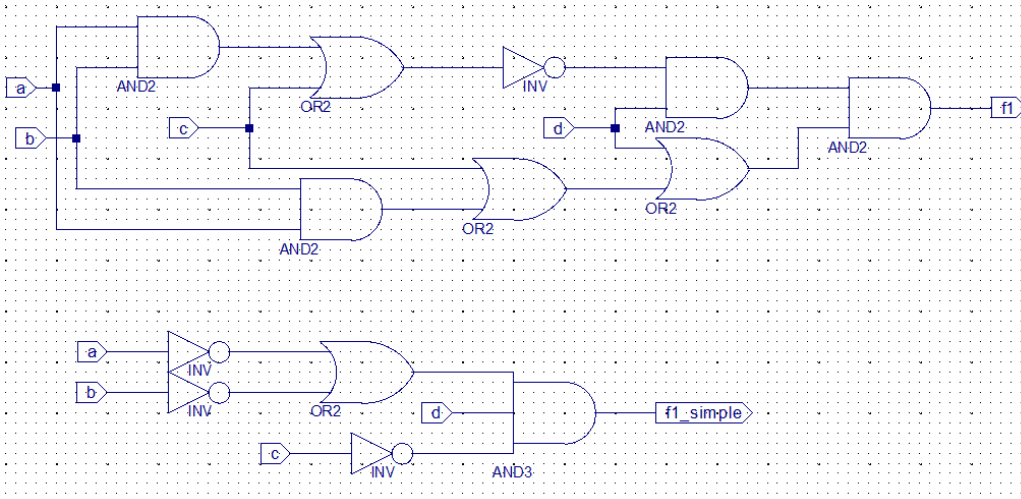
### 3. Problem 2.1 Original and simplified schematics



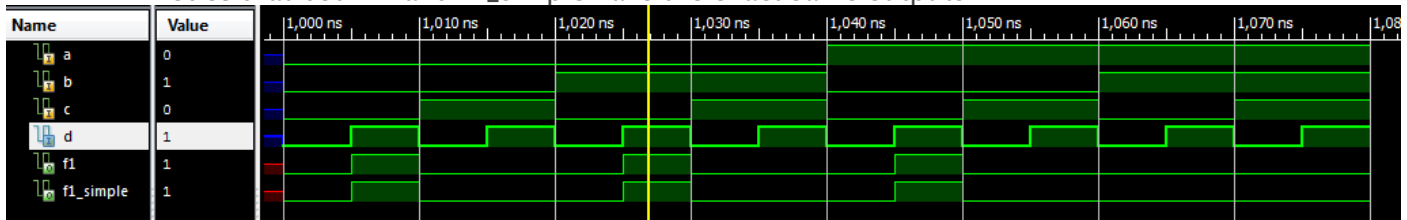
### 4. Problem 2.1 Original and simplified waveforms


Notice that both f1 and f1\_simple have the exact same outputs.


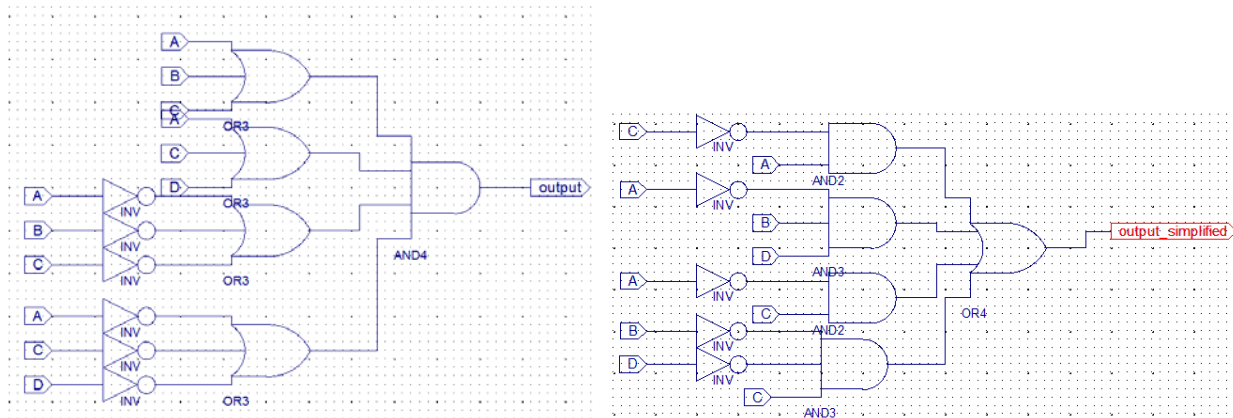
### 5. Problem 2.2 Original and simplified schematics


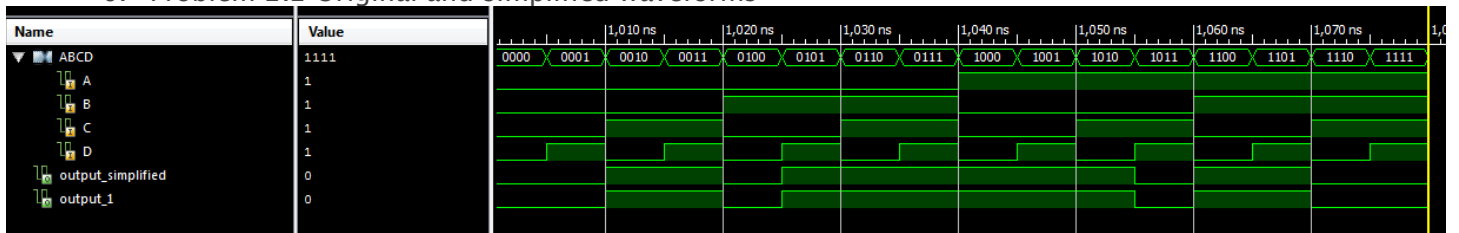
### 6. Problem 2.2 Original and simplified waveforms



## 7. Truth tables and logic minimization work (4)

### Problem 2.1


By inspection- the D anded with everything makes the second set of parentheses redundant. And so I got rid of everything inside

### Problem 2.1

A	B	C	D	$(AB+C)'D(AB+C+D)$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

### Problem 2.2

A	B	C	D	$(A+B+C)(A+C+D)(A'+B'+C')(A'+C'+D')$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

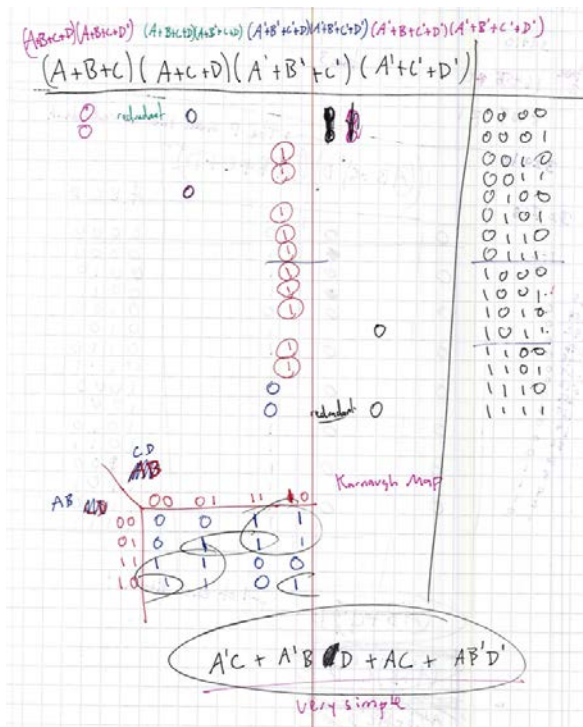

## 8. Anomalies

I had to look up online how to have 2 separate labels on the schematic actually be the same label (how to merge the nets) but other than that all was good ☺