

Taylor Cowley

Hw5

May 14 2016

ECEn 220

Chapter 9 Homework

1. Convert the following to **unsigned binary**, add the numbers together in binary, and check your result by converting it back to base-10.

3 + 7 = ? Use four bits for your operands and result.

$$\begin{array}{r} 0011 \\ + 0111 \\ \hline 1010 = 10 \end{array}$$

9 + 4 = ? Use four bits for your operands and result.

$$1001 + 0100 = 1101 = 13$$

13 + 12 = ? Use five bits for your operands and result.

$$\begin{array}{r} 01101 \\ + 1100 \\ \hline 11001 = 25 \end{array}$$

01100

2. Convert the following to **2's complement**, add the numbers together in binary. In each case first do the addition and compute a result with the same number of bits as the operands. Then, determine which operations overflow. For those overflow, first sign-extend the operands by one bit position and repeat the operations. Check your result by converting it back to base-10

3 + 7 = ? Use 4 bits for operands and result. Sign-extend them to 5 bits and do it again if overflow is detected.

$$\begin{array}{r} 0011 \quad 3 \\ + 0111 \quad 7 \\ \hline 1010 = -6 \\ \text{overflow} \end{array}$$

$$\begin{array}{r} 00011 \quad 3 \\ + 00111 \quad 7 \\ \hline 01010 = 10 \end{array}$$


5. The chapter discussed detecting overflow in 2's complement addition by looking at the sign of both operands and the sign of the result. Derive the logic equation required to detect overflow this way and draw a gate-level schematic of the resulting overflow detection circuit.

$$(A_{MSB} \oplus B_{MSB}) \cdot (A_{MSB} \oplus Cout)$$

if the 2 MSB's are the same

The carry out is different.






And

 

ECEn 220

Appendix A Homework

- A.1 Implement a 4:1 MUX using built-in gates. Draw the schematic of the corresponding circuit.
- A.2 Implement a 2:4 decoder using built-in gates. Draw the schematic of the corresponding circuit.
- A.3 Implement a 4:1 MUX using your 2:4 decoder and some built-in gates. Draw the schematic of the corresponding circuit. You can show the 2:4 decoder as a block in this schematic (no need to break it down to its constituent gates).
- A.4 Implement a 3-input XOR gate using *not*, *and*, and *or* gates. Draw the schematic of the corresponding circuit.
- A.5 Implement a 3:8 decoder using two 2:4 decoders and some gates. Draw the schematic of the corresponding circuit.
- A.6 Implement a 1-bit adder/subtractor module using built-in gates. Use the method of Section 8.7 to construct it. *-This doesn't have any meaning. I'm assuming 9.7*
- A.7 Implement an 8-bit adder/subtractor using the module you created in the previous problem.

     

A.6, A.7
no drawing
necessary

```
1 // Taylor Cowley
2 // Hw5 Appendix A problems
3 // They were horrible.
4
5 module mux_4_1(out, a, select);
6     input[3:0] a;
7     input[1:0] select;
8     output out;
9
10    wire s1_not, s0_not, and0, and1, and2, and3;
11
12    not(s1_not, select[1]);
13    not(s0_not, select[0]);
14
15    and(and0, s1_not, s0_not, a[0]);
16    and(and1, s1_not, select[0], a[1]);
17    and(and2, select[1], s0_not, a[2]);
18    and(and3, select[1], select[0], a[3]);
19    or(out, and0, and1, and2, and3);
20 endmodule
21
22
23 module decoder_2_4(out, a);
24     input[1:0] a;
25     output[3:0] out;
26
27     wire a1_not, a0_not;
28     not(a1_not, a[1]);
29     not(a0_not, a[0]);
30
31     and(out[0], a1_not, a0_not);
32     and(out[1], a1_not, a[0]);
33     and(out[2], a[1], a0_not);
34     and(out[3], a[1], a[0]);
35 endmodule
36
37
38 module mux_4_1_using_decoder(out, a, select);
39     input[3:0] a;
40     input[1:0] select;
41     output out;
42
43     wire[3:0] decoder_output;
44     wire and0, and1, and2, and3;
45
46     decoder_2_4 the_thing(decoder_output[3:0], select);
47     and(and0, a[0], decoder_output[0]);
48     and(and1, a[1], decoder_output[1]);
49     and(and2, a[2], decoder_output[2]);
50     and(and3, a[3], decoder_output[3]);
51     or(out, and0, and1, and2, and3);
52 endmodule
53
54
55 module xor_using_gates(out, a, b, c);
56     input a;
```

```
57     input b;
58     input c;
59     output out;
60
61     // I am tired of defining wires. They are not mandatory in verilog
62     nand(n_out, a, b);
63     or(o_out, a, b);
64     and(a_out, n_out, o_out);
65     nand(n_out2, a_out, c);
66     or(o_out2, a_out, c);
67     and(out, n_out2, o_out2);
68 endmodule
69
70
71 module mega_decoder(out, select);
72     input[2:0] select;
73     output[7:0] out;
74     wire[3:0] d1_out, d2_out;
75     decoder_2_4 d1(d1_out[3:0], select[1:0]);
76     decoder_2_4 d2(d2_out[3:0], select[1:0]);
77
78     not(s_2_not, select[2]);
79     and(out[0], d1_out[0], s_2_not);
80     and(out[1], d1_out[1], s_2_not);
81     and(out[2], d1_out[2], s_2_not);
82     and(out[3], d1_out[3], s_2_not);
83
84     and(out[4], d2_out[0], select[2]);
85     and(out[5], d2_out[1], select[2]);
86     and(out[6], d2_out[2], select[2]);
87     and(out[7], d2_out[3], select[2]);
88 endmodule
89
90 //Required to implement the subtractor of 9.7
91 module full_adder(sum, cout, a, b, cin);
92     // Ports
93     input a;
94     input b;
95     input cin;
96     output cout;
97     output sum;
98
99     wire a_b, b_cin, a_cin;
100
101     and(a_b, a, b);
102     and(b_cin, b, cin);
103     and(a_cin, a, cin);
104     or(cout, a_b, b_cin, a_cin);
105
106     xor(sum, a, b, cin);
107 endmodule
108
109 module add_sub(sum, cout, a, b, sub);
110     // Ports
111     input a;
112     input b;
```

```
113     input sub;
114     output cout;
115     output sum;
116
117     wire sub_not;
118     not(sub_not, sub);
119
120     xor(b_x, b, sub_not);
121     full_adder full_add(sum, cout, a, b_x, 0);
122 endmodule
123
124
125 module add_sub_8(sum, cout, a, b, sub);
126     input[7:0] a;
127     input[7:0] b;
128     input sub;
129     output cout;
130     output[7:0] sum;
131
132     not(s_not, sub);
133
134     xor(b0, b[0], s_not);
135     xor(b1, b[1], s_not);
136     xor(b2, b[2], s_not);
137     xor(b3, b[3], s_not);
138     xor(b4, b[4], s_not);
139     xor(b5, b[5], s_not);
140     xor(b6, b[6], s_not);
141     xor(b7, b[7], s_not);
142
143     full_adder add1(sum[0], cout0, a[0], b0, 0);
144     full_adder add2(sum[1], cout1, a[1], b1, cout0);
145     full_adder add3(sum[2], cout2, a[2], b2, cout1);
146     full_adder add4(sum[3], cout3, a[3], b3, cout2);
147     full_adder add5(sum[4], cout4, a[4], b4, cout3);
148     full_adder add6(sum[5], cout5, a[5], b5, cout4);
149     full_adder add7(sum[6], cout6, a[6], b6, cout5);
150     full_adder add8(sum[7], cout, a[7], b7, cout6);
151 endmodule
152
```