

Taylor Cowley
 EE 220
 May 26 2016
 Lab 08: 4x7 Segment Controller

Mod4 Verilog Code


```
module mod4(out, incr, reset, clk);
  input incr, reset, clk;
  output[1:0] out;
  reg[1:0] out_ness = 2'b00;

  always@(posedge clk)
  begin
    if(reset)
      out_ness = 2'b00;
    else if(incr)
      out_ness = out_ness + 2'b01;
    else
      out_ness = out_ness;
  end
  assign out = out_ness;
endmodule
```

Mod4 tcl file

```
isim force add clk 1 -time 0 -value 0 -time 10ns -repeat 20ns
isim force add reset 1 -time 0 -value 0 -time 30ns
isim force add incr 0 -time 0 -value 1 -time 70ns -value 0 -time 250ns
run 300ns
```

Mod4 Simulation waveform

 


Programmable Timer Verilog code

```
module test_timer(clk, out_tp, out_zero);
  output out_zero, out_tp;
  input clk;
  prog_timer yolo(clk, 0, 1, 24'd250000, counter, out_zero, out_tp);
endmodule
```

Programmable Timer UCF file

```
## clock pin for Nexys 2 Board
NET "clk" LOC = "B8";
## FX2 connector
NET "out_tp" LOC = "B4";
NET "out_zero" LOC = "A4";
```

Programmable Timer Screenshot

 

4x7 Segment Verilog Code

```
module seg4x7(seg, an, dp, dp_in, in, clk, reset, tp);
    input[15:0] in;      // The raw data. full 16 bits
    input clk;
    input[3:0] dp_in;
    input reset;
    output dp;
    output [3:0] an;
    output[6:0] seg;
    output tp;

    wire[3:0] seg_data; // In between the 16-4 mux and the decoder
    wire[1:0] an_encoded; // Comes out of mod4
    wire[3:0] an_not_inverted;
    wire[3:0] dp_inverted;
    wire zero, tp; // Will be connected to mod4's incr signal
    assign dp_inverted = ~dp_in;

    prog_timer timer(clk, reset, 1, 24'd250000, , zero, tp);

    // produces an_encoded from zero
    mod4 mod(an_encoded, zero, reset, clk);

    // Gives us a one-hot version of an
    decoder_2_4 decode(an_encoded, an_not_inverted);
    assign an = ~an_not_inverted;

    mux_16_4 right_an(seg_data, an_encoded, in[15:12], in[11:8], in[7:4], in[3:0]);

    // Changes dp_in (4-bit) to dp (1 bit) based on the an_encoded
    mux_4 a_mux(dp, an_encoded, dp_inverted);

    // Adding our seven-seg decoder schematic
    seven_seg2 seven_seg_decoder(.a(seg[0]), .b(seg[1]), .c(seg[2]), .d(seg[3]),
    .e(seg[4]), .f(seg[5]), .g(seg[6]), .n0(seg_data[0]), .n1(seg_data[1]), .n2(seg_data[2]),
    .n3(seg_data[3]));

endmodule
```

Testbench Verilog Code

```
module test(seg, an, dp, Led, sw, clk, btn, tp);
    output dp;
    output[3:0] an;
    output[6:0] seg;
    output[7:0] Led;
    input clk;
    input btn;
    input[7:0] sw;
    output tp;

    wire[15:0] go_in;
    assign Led = sw;
    assign go_in[15:12] = sw[7] ? 4'b1011 : 4'b0001;
    assign go_in[11:8] = sw[6] ? 4'b1010 : 4'b1010;
    assign go_in[7:4] = sw[5] ? 4'b1011 : 4'b1011;
    assign go_in[3:0] = sw[4] ? 4'b1110 : 4'b1000;
    seg4x7 poop(seg, an, dp, sw[3:0], go_in, clk, btn, tp);

endmodule
```

Testbench UCF file

```
## clock pin for Nexys 2 Board
NET "clk" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type = GCLK, Sch name = GCLK0
## Leds

NET "Led<0>" LOC = "J14";
NET "Led<1>" LOC = "J15";
NET "Led<2>" LOC = "K15";
NET "Led<3>" LOC = "K14";
NET "Led<4>" LOC = "E17";
NET "Led<5>" LOC = "P15";
```

```
NET "Led<6>" LOC = "F4";
NET "Led<7>" LOC = "R4";
```

Switches

```
NET "sw<0>" LOC = "G18";
NET "sw<1>" LOC = "H18";
NET "sw<2>" LOC = "K18";
NET "sw<3>" LOC = "K17";
NET "sw<4>" LOC = "L14";
NET "sw<5>" LOC = "L13";
NET "sw<6>" LOC = "N17";
NET "sw<7>" LOC = "R17";
```

Buttons

```
NET "btn" LOC = "B18";
#NET "btn<1>" LOC = "D18";
#NET "btn<2>" LOC = "E18";
#NET "btn<3>" LOC = "H13";
```

7 segment display

```
NET "seg<0>" LOC = "L18";
NET "seg<1>" LOC = "F18";
NET "seg<2>" LOC = "D17";
NET "seg<3>" LOC = "D16";
NET "seg<4>" LOC = "G14";
NET "seg<5>" LOC = "J17";
NET "seg<6>" LOC = "H14";
NET "dp" LOC = "C17";
NET "an<0>" LOC = "F17";
NET "an<1>" LOC = "H17";
NET "an<2>" LOC = "C18";
NET "an<3>" LOC = "F15";
```

```
NET "tp" LOC = "A4"; # Bank = 0, Pin name = IO_L24P_0, Type = I/O, Sch name = R-IO2
```

Anomalies

So I had my thing all coded up, but it was giving garbage values. Took me about 4.5 hours to figure out that I had things mixed up- the 2 bit an_encoded variable and the 4-bit an variable. As well as needing to invert signals for the 7 segment display that I forgot to do.