

Input				(total)	Output							
N3	N2	N1	N0		a	b	c	d	e	f	g	
0	0	0	0	0	0	0	0	0	0	0	1	
0	0	0	1	1	1	0	0	1	1	1	1	
0	0	1	0	2	0	0	1	0	0	1	0	
0	0	1	1	3	0	0	0	0	1	1	0	
0	1	0	0	4	1	0	0	1	1	0	0	
0	1	0	1	5	0	1	0	0	1	0	0	
0	1	1	0	6	0	1	0	0	0	0	0	
0	1	1	1	7	0	0	0	1	1	1	1	
1	0	0	0	8	0	0	0	0	0	0	0	
1	0	0	1	9	0	0	0	0	1	0	0	
1	0	1	0	A	0	0	0	1	0	0	0	
1	0	1	1	b	1	1	0	0	0	0	0	
1	1	0	0	C	0	1	1	0	0	0	1	
1	1	0	1	d	1	0	0	0	0	1	0	
1	1	1	0	E	0	1	1	0	0	0	0	
1	1	1	1	F	0	1	1	1	0	0	0	
					2812	D860	9004	8492	02BA	208E	1083	
High Asserted					Low Asserted							



$e = N_3'N_0 + N_3'N_2N_1' + N_2'N_1'N_0 + N_3'N_2N_1' + N_3N_2N_1' + N_3N_2N_0 + N_3N_2N_1'N_0$

$f = N_3'N_2N_1'N_0 + N_3'N_2N_1' + N_3'N_1N_0 + N_3N_2N_1'N_0$


$c = N_3'N_2N_1'N_0 + N_3'N_2N_1' + N_3N_2N_0 + N_3N_2N_1'N_0$

## Procedure
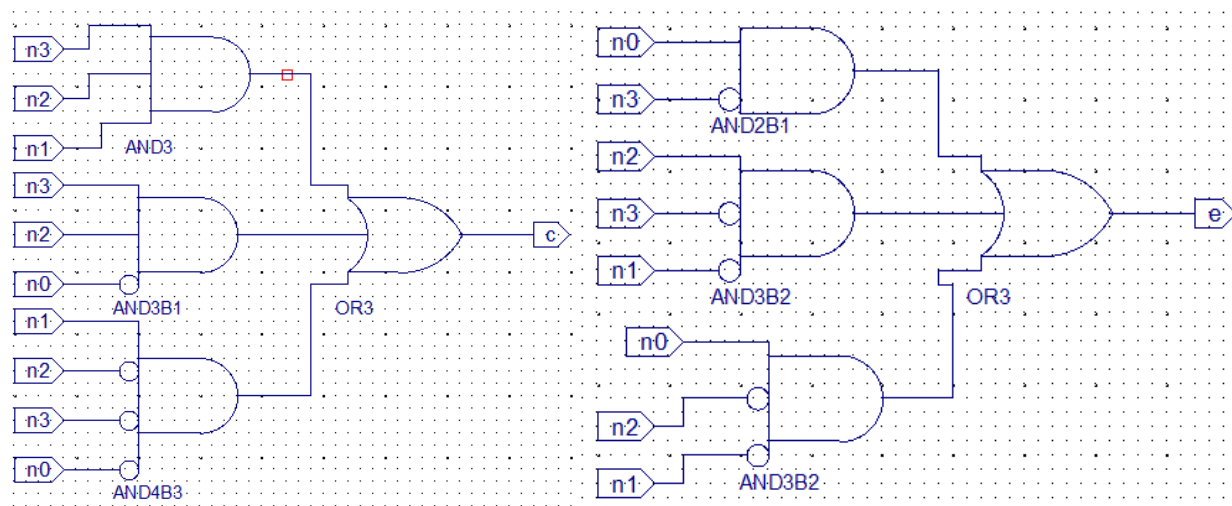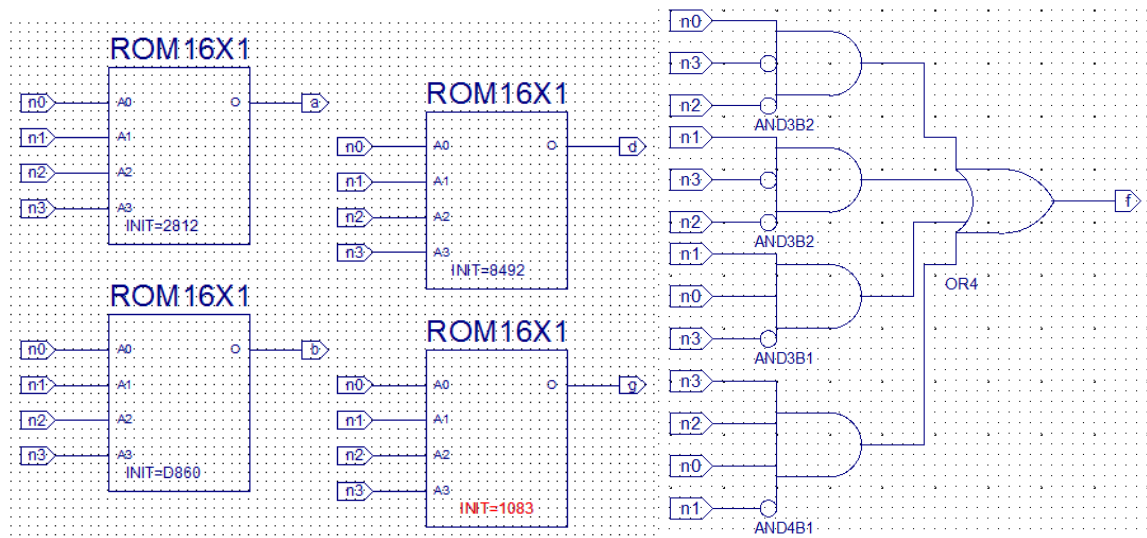
### ROM schematic and Combinational Logic Schematic



### Seven Segment Decoder Schematic

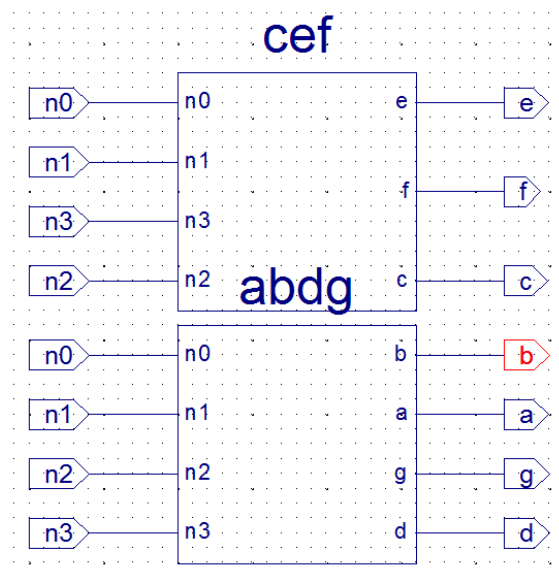

## TCL File for simulation

```

isim force add n3 0
isim force add n2 0
isim force add n1 0
isim force add n0 0
run 5ns
isim force add n0 1
run 5ns
isim force add n1 1
isim force add n0 0
run 5ns
isim force add n0 1
run 5ns
isim force add n2 1
isim force add n1 0
isim force add n0 0
run 5ns

```

```

isim force add n0 1
run 5ns
isim force add n1 1
isim force add n0 0
run 5ns
isim force add n0 1
run 5ns
isim force add n3 1
isim force add n2 0
isim force add n1 0
isim force add n0 0
run 5ns
isim force add n0 1
run 5ns
isim force add n1 1
isim force add n0 0


```

```


run 5ns
isim force add n0 1
run 5ns
isim force add n2 1
isim force add n1 0
isim force add n0 0
run 5ns
isim force add n0 1
run 5ns
isim force add n1 1
isim force add n0 0
run 5ns
isim force add n0 1
run 5ns

```
 
## Simulation waveform for top-level seven-segment schematic



## Test Bench Schematic

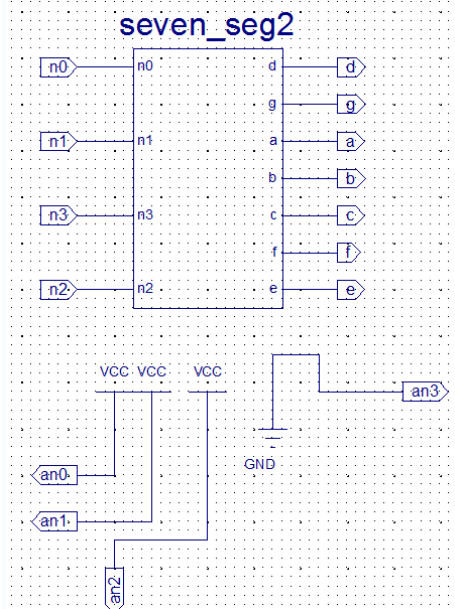

## Test Bench UCF

```

## Switches
NET "n0" LOC = "L14";
NET "n1" LOC = "L13";
NET "n2" LOC = "N17";
NET "n3" LOC = "R17";
## 7 segment display
NET "a" LOC = "L18";
NET "b" LOC = "F18";
NET "c" LOC = "D17";
NET "d" LOC = "D16";
NET "e" LOC = "G14";
NET "f" LOC = "J17";
NET "g" LOC = "H14";
NET "an0" LOC = "F17";
NET "an1" LOC = "H17";
NET "an2" LOC = "C18";
NET "an3" LOC = "F15";

```

**Anomalies (bugs, problems, and suggestions)(5pts possible)**

Well the first time I did the K-maps, I did it all correct, but I did not implement the schematic according to the k-map. So I had to redo the schematic. Also, I got confused on how to initialize the ROM to the proper value- I was reading the truth table backwards to make the Hexadecimal values.