

Taylor Cowley

Lab 10: Designing the LC3 Datapath (LC3 Functional Units)


Why do these labs have 2 separate titles?

June 13 2016

EAB Verilog file

```
1 // The EAB. Which includes
2 // The ADDR2MUX
3 // ADDR1MUX
4 // ADDER
5 // Sign extension before the addr2mux
6
7 module EAB(eabOut, PC, Ra, selEAB1, selEAB2, IR);
8     output[15:0] eabOut;
9     input[15:0] PC;
10    input[15:0] Ra;
11    input selEAB1;
12    input[1:0] selEAB2;
13    input[10:0] IR;
14
15    wire[15:0] adder_input1, adder_input2;
16
17    // ADDR1MUX - If 1, Ra. If 2, PC
18    // No sign extension needed because Ra and PC are both 16 bits
19    assign adder_input1 = selEAB1 ? Ra : PC ;
20
21    // ADDR2MUX - If 3, IR[10:0]
22    //     If 2, IR[8:0]
23    //     If 1, IR[5:0]
24    //     If 0, 0
25    //     All need to be sign-extended to 16 bits
26    assign adder_input2 = (selEAB2 == 2'b11) ? {5{IR[10]}} , IR[10:0] :
27                          (selEAB2 == 2'b10) ? {7{IR[8] }} , IR[8:0] :
28                          (selEAB2 == 2'b01) ? {10{IR[5] }} , IR[5:0] :
29                          16'h0000;
30    assign eabOut = adder_input1 + adder_input2;
31 endmodule
32
```

EAB Simulation waveform

 


MARMux Verilog file

```

1 // This is the MARMUX.
2 // it only has the MARMUX in it
3 module MARMUX(MARMuxOut, selMAR, IR, eabOut);
4     output[15:0] MARMuxOut;
5     input selMAR;
6     input[7:0] IR;
7     input[15:0] eabOut;
8
9     // If 1, a zero-extended IR. If 0, eabOut.
10    assign MARMuxOut = selMAR ? {8'h00, IR[7:0]} : eabOut;
11
12 endmodule
13

```

MARMux Simulation waveform

 


PC Verilog file

```

1 // This is PC.
2 // It includes PCMUX, the PC itself, and a +1 adder
3 module PC(PC, selPC, eabOut, ldPC, clk, reset, Buss);
4     output[15:0] PC;
5     input[1:0] selPC;
6     input[15:0] eabOut;
7     input ldPC;
8     input clk;
9     input reset;
10    input[15:0] Buss;
11
12
13    // This implements PCMUX.
14    // 00-PC+1
15    // 01-eabOut
16    // 10-Buss
17    // 11-0xFF just for fun (not authorized)
18    wire[15:0] pcmux_out;
19    assign pcmux_out = (selPC==2'b00) ? PC + 1:
20                      (selPC==2'b01) ? eabOut:
21                      (selPC==2'b10) ? Buss:
22                      16'hFF;
23
24    register pc_register(PC, clk, pcmux_out, reset, ldPC);
25
26 endmodule

```

PC Simulation waveform

 


IR Verilog file

```

1 // This is the IR.
2 // It is pretty boring and doesn't contain much
3 module IR(IR, ldIR, clk, reset, Buss);
4     output[15:0] IR;
5     input clk, reset, ldIR;
6     input[15:0] Buss;
7
8     register ir_register(IR, clk, Buss, reset, ldIR);
9 endmodule
10

```

IR Simulation waveform

 


NZP Verilog file

```

1 // This is the NZP module. It's pretty simple
2 module NZP(N, Z, P, flagWE, clk, reset, Buss);
3     output N, Z, P;
4     input flagWE, clk, reset;
5     input[15:0] Buss;
6
7     // If the MSB of Buss is set, we are negative
8     register_1bit N_register(N, clk, Buss[15], reset, flagWE);
9     // If ANY bit of Buss is set but the MSB, we are positive
10    register_1bit P_register(P, clk, ((Buss & ~Buss[15])), reset, flagWE);
11    // All bits need to be zero = none can be one
12    register_1bit Z_register(Z, clk, ~(Buss), reset, flagWE);
13
14 endmodule
15
16 module register_1bit(dout, clk, din, reset, load);
17     input clk, reset, load;
18     input din;
19     output reg dout;
20
21     always @(posedge clk)
22         if (reset) dout <= 1'd0;
23         else if (load) dout <= din;
24 endmodule
25

```

NZP Simulation waveform

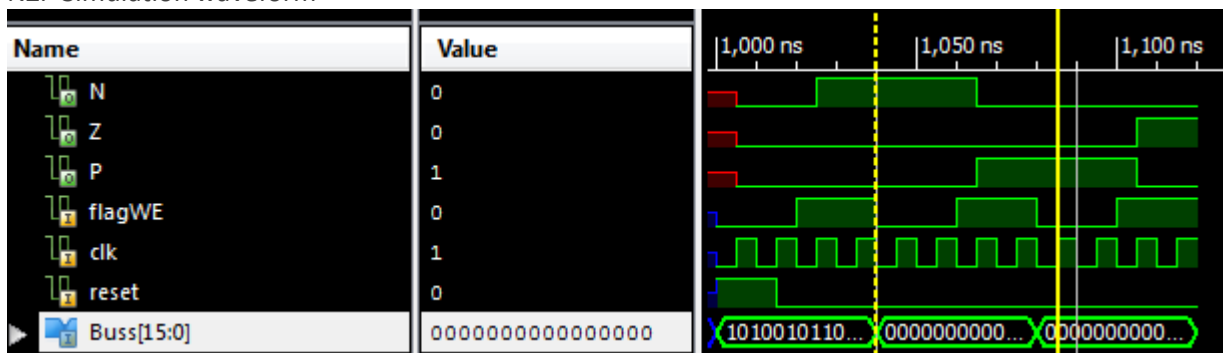


ALU Verilog file

```

1 // An ALU. It says it is the same one we already did
2 // 00 = A
3 // 01 = ADD
4 // 10 = AND
5 // 11 = NOT A
6 module ALU(aluOut, aluControl, IR, Rb, Ra);
7     output[15:0] aluOut;
8     input[1:0] aluControl;
9     input[5:0] IR;
10    input[15:0] Rb, Ra;
11
12    // First we need to do SR2MUX - 0 means Rb, 1 means IR[4:0]
13    wire[15:0] sr2mux;
14    assign sr2mux = IR[5] ? {{11{IR[4]}},IR[4:0]} : Rb;
15
16    assign aluOut = (aluControl==2'b00) ? Ra :
17                    (aluControl==2'b01) ? Ra + sr2mux :
18                    (aluControl==2'b10) ? Ra & sr2mux :
19                    ~Ra;
20 endmodule
21

```

ALU Simulation waveform

 


ts_driver Verilog file

```

1 // Copy-pasted from learning suite?
2 module ts_driver ( din, dout, ctrl );
3     input [15:0] din;
4     input ctrl;
5     output [15:0] dout;
6
7     assign dout = (ctrl)? din:(16'bZZZZZZZZZZZZZZZZ);
8 endmodule
9

```

ts_driver Simulation waveform

 


RegFile Verilog file

```

1 // Here we shall do the Reg file.
2 // It doesn't look too hard to redo so let's redo it
3
4 module REG_FILE(Rb, Ra, DR, SR1, SR2, regWE, clk, reset, Buss);
5     output[15:0] Rb, Ra;
6     input[2:0] DR, SR1, SR2;
7     input regWE, clk, reset;
8     input[15:0] Buss;
9
10    wire[15:0] r0,r1,r2,r3,r4,r5,r6,r7;
11    // They are only written when WE is on and that register is selected
12    register reg0(r0, clk, Buss, reset, regWE&(DR==3'b000));
13    register reg1(r1, clk, Buss, reset, regWE&(DR==3'b001));
14    register reg2(r2, clk, Buss, reset, regWE&(DR==3'b010));
15    register reg3(r3, clk, Buss, reset, regWE&(DR==3'b011));
16    register reg4(r4, clk, Buss, reset, regWE&(DR==3'b100));
17    register reg5(r5, clk, Buss, reset, regWE&(DR==3'b101));
18    register reg6(r6, clk, Buss, reset, regWE&(DR==3'b110));
19    register reg7(r7, clk, Buss, reset, regWE&(DR==3'b111));
20
21    assign Ra = (SR1==3'b000) ? r0 :
22                (SR1==3'b001) ? r1 :
23                (SR1==3'b010) ? r2 :
24                (SR1==3'b011) ? r3 :
25                (SR1==3'b100) ? r4 :
26                (SR1==3'b101) ? r5 :
27                (SR1==3'b110) ? r6 :
28                r7;
29
30    assign Rb = (SR2==3'b000) ? r0 :
31                (SR2==3'b001) ? r1 :
32                (SR2==3'b010) ? r2 :
33                (SR2==3'b011) ? r3 :
34                (SR2==3'b100) ? r4 :
35                (SR2==3'b101) ? r5 :
36                (SR2==3'b110) ? r6 :
37                r7;
38 endmodule
39

```

RegFile Simulation waveform

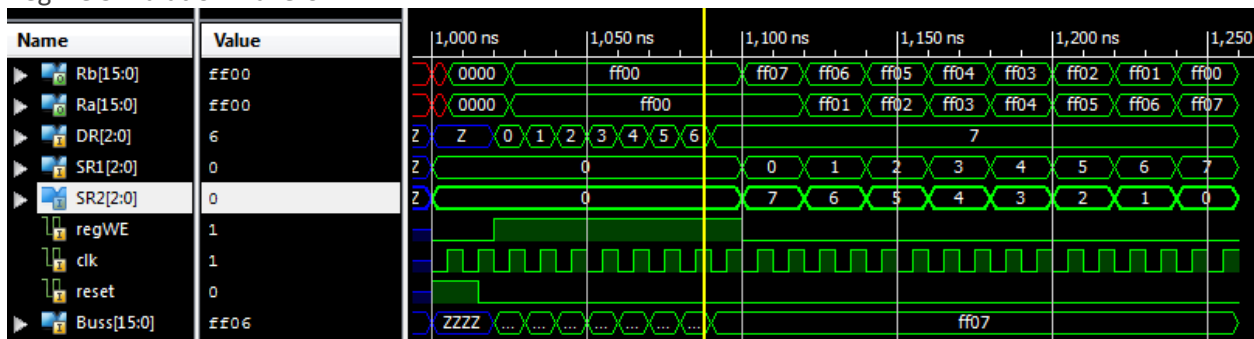

Anomalies (bugs, problems, and suggestions)(5pts possible)

So just realizing that I had to trust the basic modules- they aren't doing anything special! Then it was easy to code up. And VIM is much nicer to code Verilog into than the Xilinx editor. In case you were wondering.