

Taylor Cowley
Lab 05: Arithmetic Logic Unit
May 17 2016

Full Adder Verilog and .tcl files

```
module full_adder(sum, cout, a, b, cin);  
    // Ports  
    input a;  
    input b;  
    input cin;  
    output cout;  
    output sum;  
  
    wire a_b, b_cin, a_cin;  
  
    and(a_b, a, b);  
    and(b_cin, b, cin);  
    and(a_cin, a, cin);  
    or(cout, a_b, b_cin, a_cin);  
  
    xor(sum, a, b, cin);  
endmodule
```

```
isim force add a 0  
isim force add b 0  
isim force add cin 0  
run 5ns  
isim force add cin 1  
run 5ns  
isim force add cin 0  
isim force add b 1  
run 5 ns  
isim force add cin 1  
run 5 ns  
isim force add a 1  
isim force add b 0  
isim force add cin 0  
run 5 ns  
isim force add cin 1  
run 5 ns  
isim force add cin 0  
isim force add b 1  
run 5 ns  
isim force add cin 1  
run 5 ns
```

4:1 Mux Verilog and .tcl files

```
module mux_2(q, sel, a, b);  
    input a;  
    input b;  
    input sel;  
    output q;  
  
    wire a1, a2, selbar;  
  
    not(selbar, sel);  
    and(a1, selbar, a);  
    and(a2, sel, b);  
    or(q, a1, a2);  
endmodule
```

```
input d;  
input[1:0] sel;  
output q;
```

```
wire a_or_b, c_or_d;
```

```
mux_2 M0(a_or_b, sel[0], a, b);
```

```
// The LSB selects between a or b
```

```
mux_2 M1(c_or_d, sel[0], c, d);
```

```
// and c or d
```

```
mux_2 M2(q, sel[1], a_or_b, c_or_d);
```

```
the MSB selects between those 2
```

```
endmodule
```

.tcl file

```
isim force add sel 00  
isim force add a 0  
isim force add b 1  
isim force add c 1
```

```
module mux_4(q, sel[1:0], a, b, c, d);  
    input a;  
    input b;  
    input c;
```

```

isim force add d 1
run 5 ns
isim force add sel 01
run 5 ns
isim force add sel 10
run 5 ns
isim force add sel 11
run 5 ns

```

```

isim force add sel 00
isim force add a 1
isim force add b 0
isim force add c 1
isim force add d 1
run 5 ns
isim force add sel 01
run 5 ns
isim force add sel 10
run 5 ns
isim force add sel 11
run 5 ns

```

```

isim force add sel 00
isim force add a 1

```

```

isim force add b 1
isim force add c 0
isim force add d 1
run 5 ns
isim force add sel 01
run 5 ns
isim force add sel 10
run 5 ns
isim force add sel 11
run 5 ns


```

```


isim force add sel 00
isim force add a 1
isim force add b 1
isim force add c 1
isim force add d 0
run 5 ns
isim force add sel 01
run 5 ns
isim force add sel 10
run 5 ns
isim force add sel 11
run 5 ns

```

4:1 Mux simulation waveform

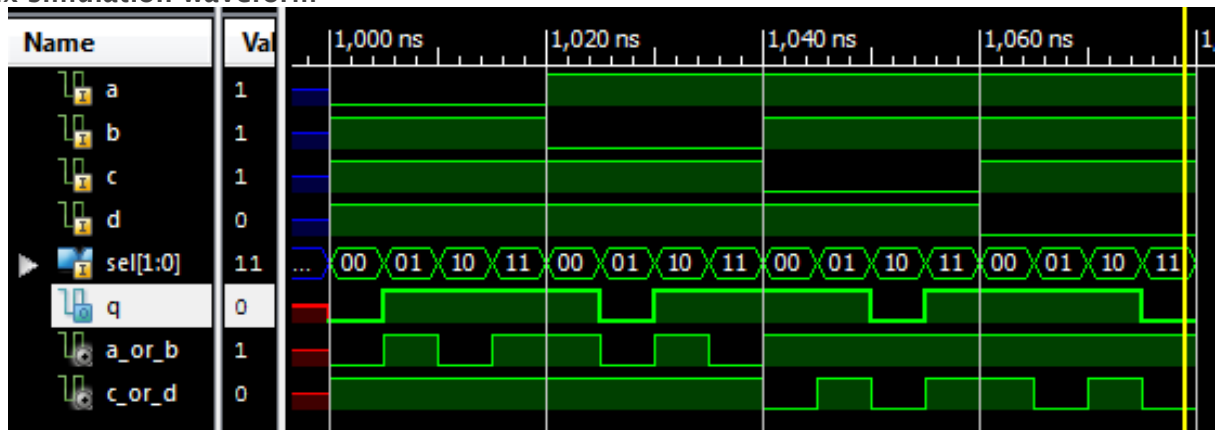


Full Adder simulation waveform

 

1 bit ALU Verilog code and .tcl file

<i>module alu(out, cout,</i>	<i>isim force add c 1</i>	<i>isim force add b 1</i>
<i>c[1:0], a, b, cin);</i>	<i>isim force add d 1</i>	<i>isim force add c 0</i>
<i>// Ports</i>	<i>run 5 ns</i>	<i>isim force add d 1</i>
<i>input a;</i>	<i>isim force add sel 01</i>	<i>run 5 ns</i>
<i>input b;</i>	<i>run 5 ns</i>	<i>isim force add sel 01</i>
<i>input cin;</i>	<i>isim force add sel 10</i>	<i>run 5 ns</i>
<i>input[1:0] c;</i>	<i>run 5 ns</i>	<i>isim force add sel 10</i>
<i>output cout;</i>	<i>isim force add sel 11</i>	<i>run 5 ns</i>
<i>output out;</i>	<i>run 5 ns</i>	<i>isim force add sel 11</i>
		<i>run 5 ns</i>
<i>wire a_b, a_not,</i>	<i>isim force add sel 00</i>	
<i>sum;</i>	<i>isim force add a 1</i>	<i>isim force add sel 00</i>
	<i>isim force add b 0</i>	<i>isim force add a 1</i>
<i>and(a_b, a, b);</i>	<i>isim force add c 1</i>	<i>isim force add b 1</i>
<i>not(a_not, a);</i>	<i>isim force add d 1</i>	<i>isim force add c 1</i>
<i>full_adder add(sum,</i>	<i>run 5 ns</i>	<i>isim force add d 0</i>
<i>cout, a, b, cin);</i>	<i>isim force add sel 01</i>	<i>run 5 ns</i>
	<i>run 5 ns</i>	<i>isim force add sel 01</i>
<i>mux_4 select(out,</i>	<i>isim force add sel 10</i>	<i>run 5 ns</i>
<i>c[1:0], a, sum, a_b, a_not);</i>	<i>run 5 ns</i>	<i>isim force add sel 10</i>
<i>endmodule</i>	<i>isim force add sel 11</i>	<i>run 5 ns</i>
	<i>run 5 ns</i>	<i>isim force add sel 11</i>
<i>isim force add sel 00</i>	<i>isim force add sel 00</i>	<i>run 5 ns</i>
<i>isim force add a 0</i>	<i>isim force add a 1</i>	
<i>isim force add b 1</i>		

1 Bit ALU simulation waveform

 

4 bit ALU Verilog code and .tcl file

```

module alu_4(out[3:0], cout, c[1:0], a[3:0], b[3:0], cin);
// Ports
input[3:0] a;
input[3:0] b;
input cin;
input[1:0] c;
output cout;
output[3:0] out;

```

```
wire carry0, carry1, carry2;
```

```
alu alu0(out[0], carry0, c[1:0], a[0], b[0], cin);
alu alu1(out[1], carry1, c[1:0], a[1], b[1], carry0);
alu alu2(out[2], carry2, c[1:0], a[2], b[2], carry1);
alu alu3(out[3], cout, c[1:0], a[3], b[3], carry2);
```

```
endmodule
```

```
isim force add a 0000 -time 0 -value 0001 -time 5 ns -value 0010 -time 10 ns -value 0011 -time 15 ns
-value 0100 -time 20 ns -value 1000 -time 25 ns -value 1100 -time 30 ns -value 1111 -time 35 ns -
repeat 50 ns
isim force add b 0000 -time 0 -value 0001 -time 50 ns -value 0010 -time 100 ns -value 0011 -time 150
ns -value 0100 -time 200 ns -value 1000 -time 205 ns -value 1100 -time 300 ns -value 1111 -time 350
ns -repeat 500 ns
isim force add cin 0 -time 0 -value 1 -time 500 ns -repeat 1000
isim force add c 00 -time 0 -value 01 -time 1000 ns -value 10 -time 2000 ns -value 11 -time 3000 ns
run 4000 ns
```

4 bit ALU simulation waveform- both entire thing and more useful snapshot



4 bit ALU UCF file

```
## Leds
NET "out<0>" LOC = "J14"
NET "out<1>" LOC = "J15";
```

```
NET "out<2>" LOC = "K15";  
NET "out<3>" LOC = "K14";  
#NET "Led<4>" LOC = "E17";  
#NET "Led<5>" LOC = "P15";  
#NET "Led<6>" LOC = "F4";  
NET "cout" LOC = "R4";
```

Switches

```
NET "b<0>" LOC = "G18";  
NET "b<1>" LOC = "H18";  
NET "b<2>" LOC = "K18";  
NET "b<3>" LOC = "K17";  
NET "a<0>" LOC = "L14";  
NET "a<1>" LOC = "L13";  
NET "a<2>" LOC = "N17";  
NET "a<3>" LOC = "R17";
```

Buttons

```
NET "cin" LOC = "B18";  
NET "c<0>" LOC = "E18";  
NET "c<1>" LOC = "H13";
```

Anomalies (bugs, problems, and suggestions)

I had major issues with the .tcl file for the 4-bit ALU. I wanted to test most of the possibilities, but I could not hard code everything like I had been doing. I forgot to put the dash in front of value, I had the timing all wrong, but I eventually was able to work it out nicely. And it tested perfectly. 😊