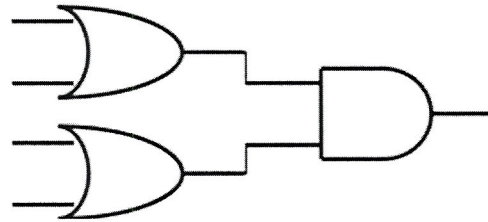


Taylor Cowley
EE220 HW 3
May 6


ECEn 220 Chapter 6 Homework




1. Implement the schematic above using only NOR gates.



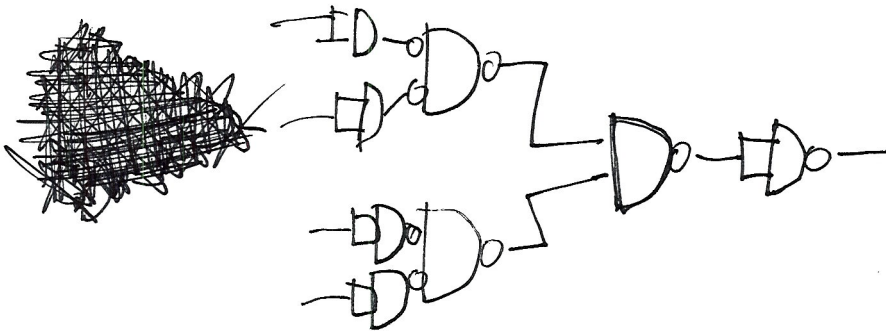
2. Implement the schematic above using only NAND gates.




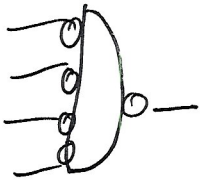
3. Assume you have been given the assignment to design a function to determine whether the value of a 4-bit Boolean value is NOT equal to zero. A 4-bit value is zero if all of its individual bits are zero. The output of this function should be TRUE when the value of the 4-bit value is NOT zero. Draw a single-gate schematic which implements this function. Use the correct symbol and justify your answer.



if all are zero, it prints out false

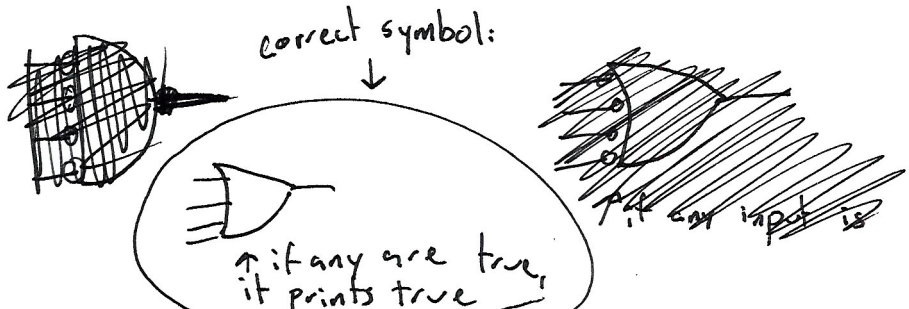


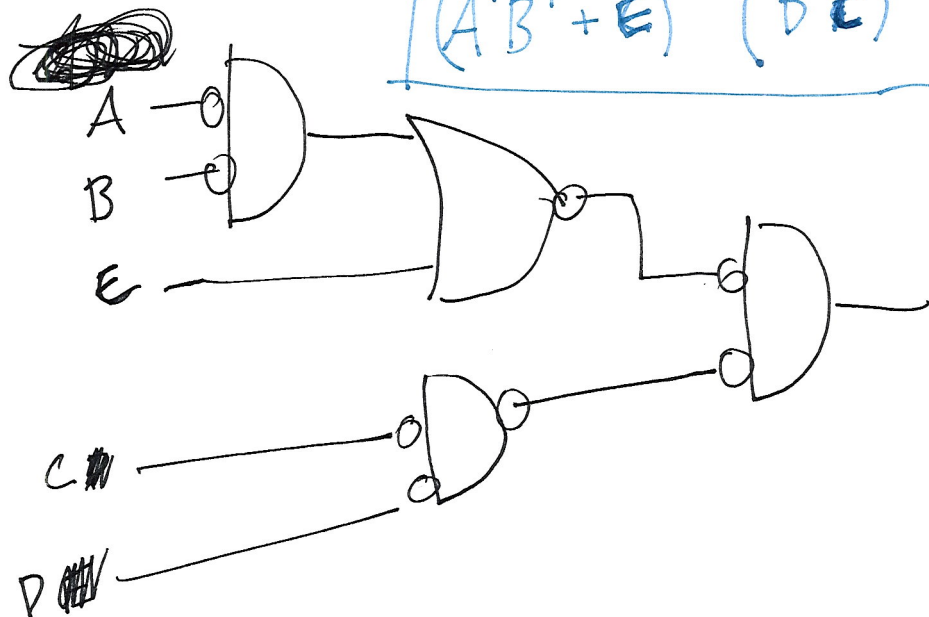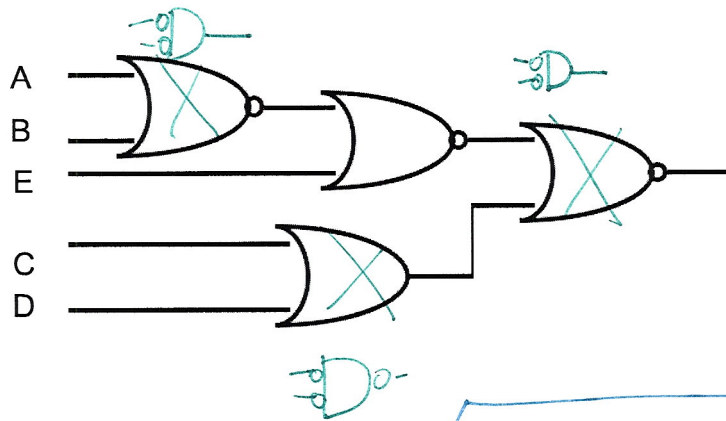4. Bubble match the schematic below to have a non-inverted output. Then, write the logic function the circuit implements by inspection (no simplification is necessary).



$$(A'B' + E)'' (D'C')''$$

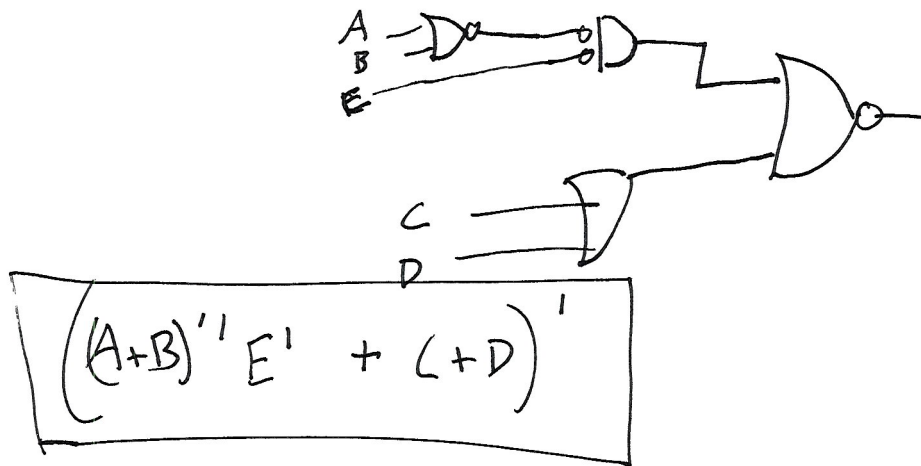5. Bubble match the schematic in Question 4 to have an inverted output. Then, write the logic function the circuit implements by inspection.



6. Use DeMorgan's to verify that your answers to the previous two problems are equivalent.

$$(A'B' + E)'' (D'C')'' = ? \quad \text{[scribbled out]} \quad ((A+B)'' E' + (C+D))'$$

$$((A+B)'' E' + (C+D))' \quad \text{---} \quad ''$$

ECEn 220

Chapter 7 Homework

1. Using a KMap, prove the following equality is true.

$$AB'C' + BC' = AC' + BC'$$

Black

Pink

		A	
		0	1
BC	00	0 0	1 1
	01	0 0	0 0
	11	0 0	0 0
	10	1 1	1 1

They are the same!

2. How many prime implicants and essential prime implicants are in the K-map below? Circle all prime implicants.

CD \ AB	AB			
	00	01	11	10
00	1	1	0	1
01	1	1	1	1
11	0	1	0	1
10	1	1	0	1

Prime Implicants:

Essential Prime Implicants:

7

3

7. Consider the following problem: $F(A,B,C,D) = \sum m(0,1,5,6,7,10,13) + \sum d(2,4,9,12,14)$. Identify and write all the prime implicant and essential prime implicant terms in its KMap. Then clearly mark (using color) the essential prime implicants.

AB \ CD	00	01	11	10
00	1	X	X	0
01	1	1	1	X
11	0	1	0	0
10	X	1	X	1

Prime Implicants: 7

Essential Prime Implicants: 2

8. Write the minimum SOP solution to the KMap above. If multiple minimum solutions exist, show all of them.

AB \ CD	00	01	11	10
00	1	X	X	0
01	1	1	1	X
11	0	1	0	0
10	X	1	X	1

AB \ CD	00	01	11	10
00	1	X	X	0
01	1	1	1	X
11	0	1	0	0
10	X	1	X	1

AB \ CD	00	01	11	10
00	1	X	X	0
01	1	1	1	X
11	0	1	0	0
10	X	1	X	1

$$F = CD' + A'B + A'C' + C'D \quad F = CD' + A'B + A'C' + BC' \quad F = CD' + A'B + A'D' + C'D$$

AB \ CD	00	01	11	10
00				
01				
11				
10				

F =

9. Consider the following problem: $F(A,B,C,D) = \sum m(0,2,3,4,5,6,7) + \sum d(1,8,9,10)$. Find the minimum SOP and POS solutions to this problem. If multiple minimum solutions exist, show all of them.

		AB			
		00	01	11	10
CD	00	1	1	0	X
	01	X	1	0	X
	11	1	1	0	0
	10	1	1	0	X

EASY. $F = A'$